


FEDERAL UNIVERSITY OF TECHNOLOGY MINNA
DEPARTMENT OF INDUSTRIAL AND TECHNOLOGY EDUCATION
FIRST SEMESTER EXAMINATION 2018/2019 SESSION

Course Title: Circuit Theory. Course Code: ITE 353


Instruction: Answer 3 Questions only. Time: 1½ hours

(1) Define the following terms:

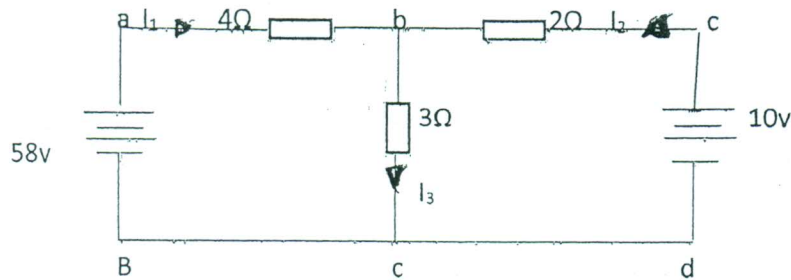- (a) Node (ii) Mesh (iii) Linear Network (iv) Bilateral Network (v) Distributed Network.
 (b) Use Kirchhoff's law to determine the current and voltage drop in the network below.




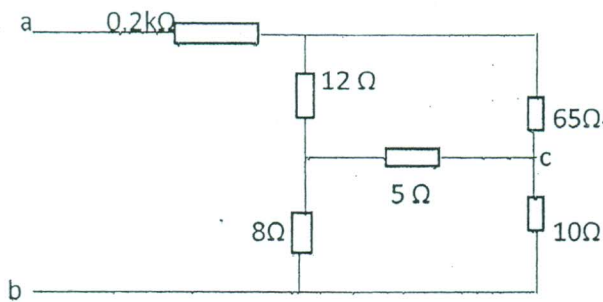- (2) (a) Explain the difference between Kirchhoff's Current and Voltage laws.
 (b) Reduce the current below to a single equivalent resistance.



(3) (a) Explain Thevenin's Theorem of voltage and resistance.

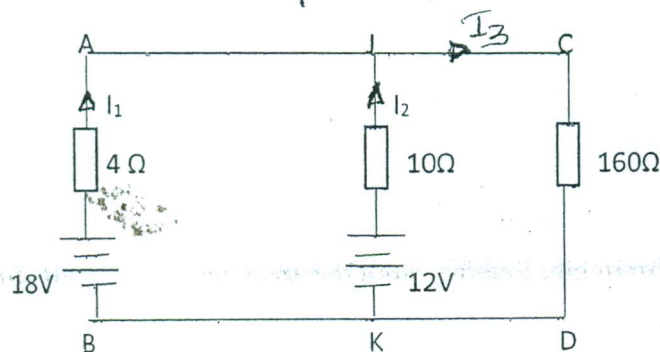- (b) In the circuit below, use superposition law to calculate the current flowing in each resistors and determine the pd across point J and K



- (4) (a) Using relevant circuit diagram, explain the steps involve when using Thevenin's Theorem to determine the current in any branch of an active network.